











Electrical Circuit

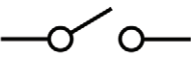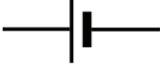Electricity flows in a circuit from the negative pole of a battery to its positive pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit.

 battery	 closed switch	 open switch	 cell	 voltmeter
 buzzer	 bulb	 bulb	 motor	 wire

Label the circuit below.

